

THYRISTORS


Lecture 7

OVERVIEW


- Basic structure of Thyristor
- Working principles of Thyristor
- Forward Breakover Voltage
- Holding and switching current
- The Silicon-Controlled Rectifier (SCR).
- SCR Characteristics and Rating
- SCR Applications

BASIC STRUCTURE

- **Definition:** The device acts as a switch and remains off until the forward voltage reaches a certain value; then it turns on and conducts. Conduction continues until the current is reduced below a specified value.
- **Basics:**
 - Two terminals: Anode & Cathode
 - 4-layer device (4 semiconductor layers)
 - *pnpn* structure
 - Three *pn* junction
 - Known as **Shokley** diode & SUS (Silicon Unilateral Switch)

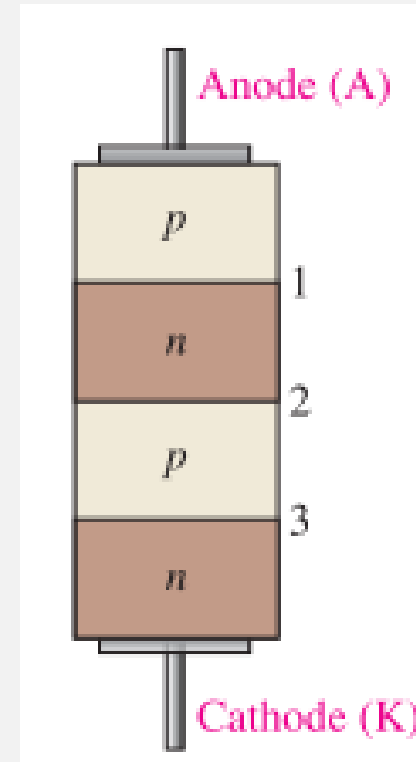



Schematic symbol

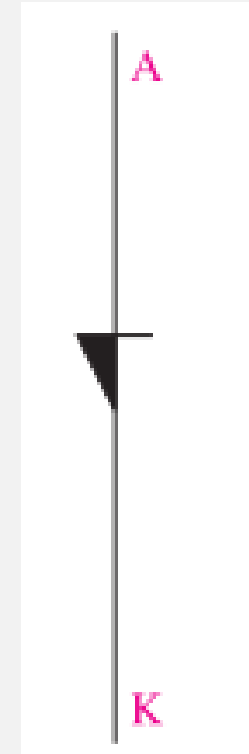

Schematic symbol

BASIC STRUCTURE

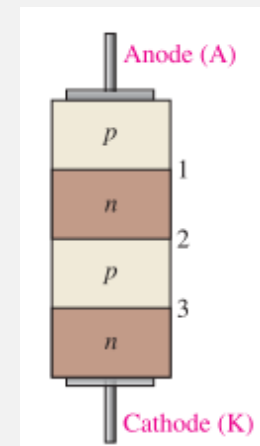
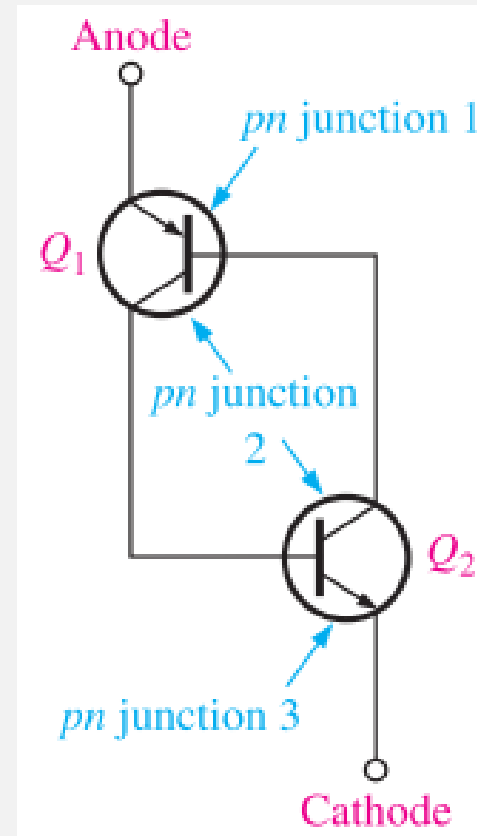
- Thyristor equivalent circuit::
 - *pnp* and *npn* transistors
 - Upper *pnp* layer as Q_1 and lower *npn* layer from Q_2
 - Middle layer shared by both transistors



WORKING PRINCIPLE

Positive bias voltage applied to the anode with respect to cathode

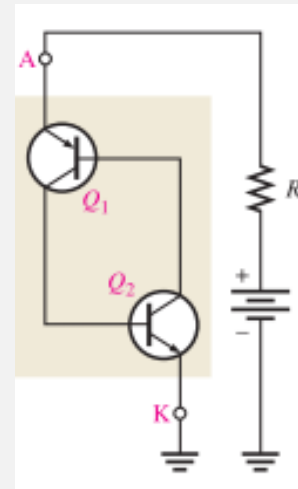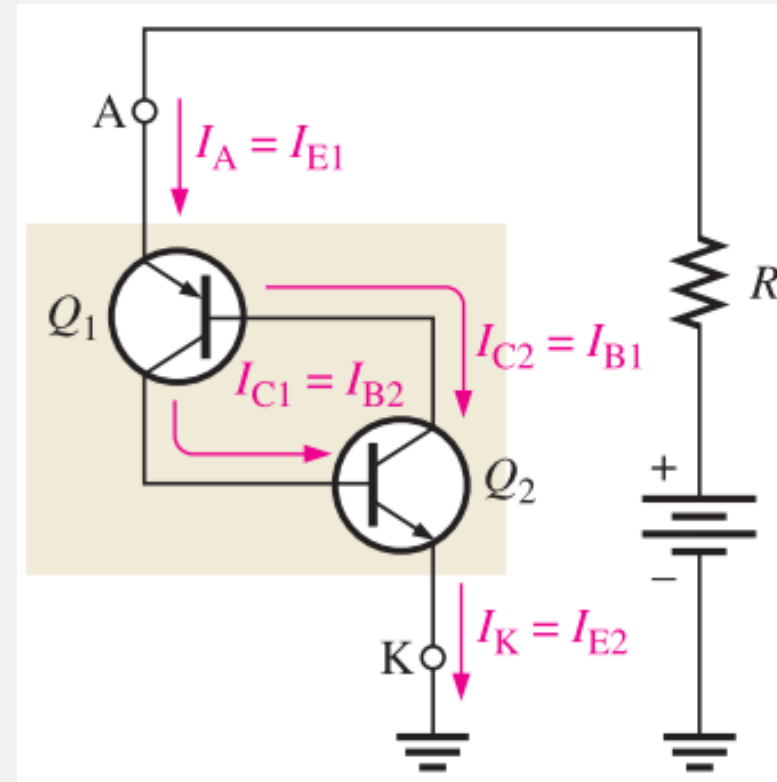- The base-emitter junction Q_1 & Q_2 are forward-biased
- Common base-collector junction (pn) is reverse-biased
- At low-bias level → Anode current is little → It is in the **OFF** state or forward-blocking region





FORWARD-BREAKOVER VOLTAGE

□ Forward-blocking region (forward bias):

- Device has a very high forward resistance (ideally an open)
- Device is in **OFF** state, acts as an open switch
- Exist from: $V_{AK} = 0\text{ V}$ to value $V_{AK} = V_{BR(F)}$ (called *forward-breakover voltage*)
- As V_{AK} is increased \rightarrow Anode current I_A gradually increases.
- When I_A reaches I_S (Switching current) $\rightarrow V_{AK} = V_{BR(F)}$


□ Forward-conduction region:

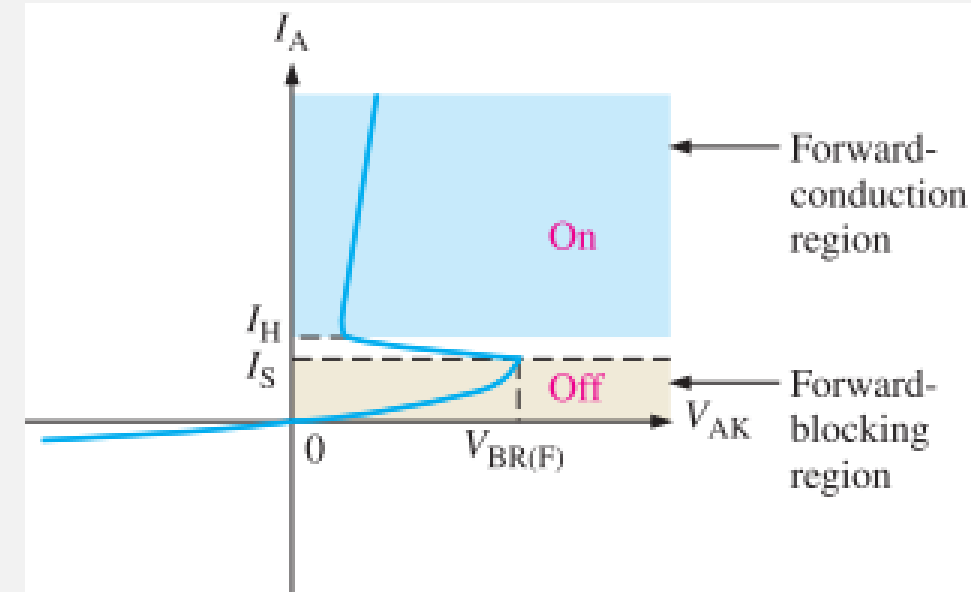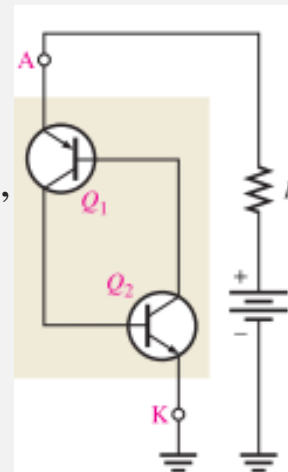- When internal transistor structures become saturated, V_{AK} suddenly decreases to low value
- The device is **ON** state and acts as a closed switch



HOLDING AND SWITCHING CURRENT


- Holding Current (I_H)
 - When the 4-layer diode (Thyristor) is in the **ON** state, conduction continues till anode current is reduced below a specified level, called holding current " I_H "
 - Device switches to **OFF** state and enters the forward-blocking region, once I_A falls below I_H .
- Switching current (I_S)
 - Anode current value where the device switches from the forward-blocking-region (**OFF**) to the forward-conduction region (**ON**)
 - The value is always less than the holding current (I_H)

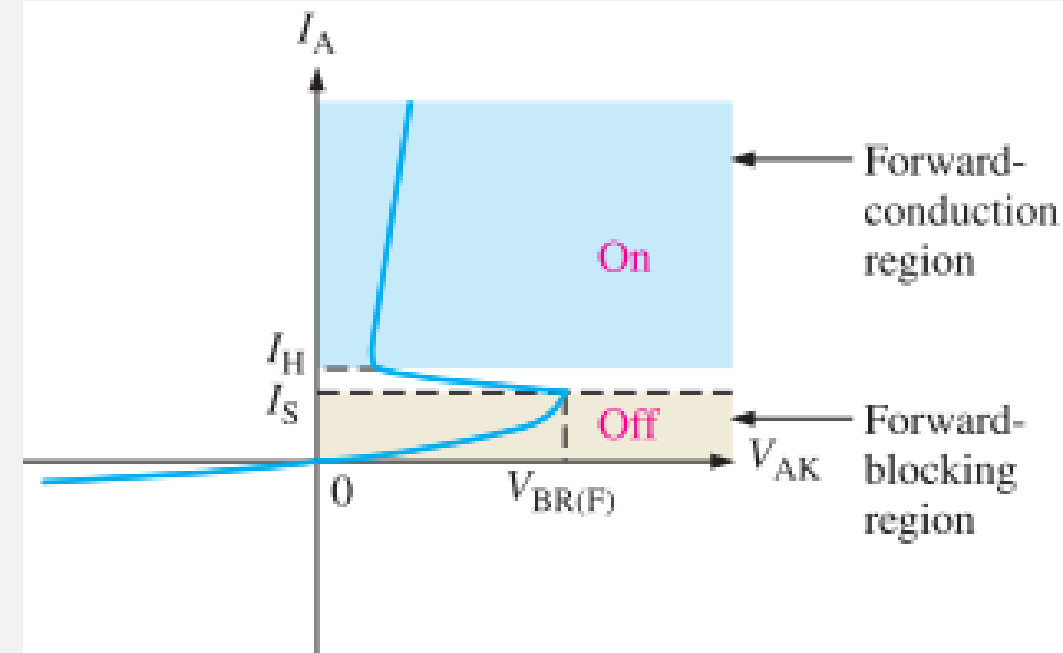

SHOCKLEY DIODE APPLICATION



Relaxation oscillator

- When the switch is closed, the capacitor charges through R until its voltage reaches the forward breakover voltage of the 4-layer diode.
- When voltage reaches $V_{BR(F)}$, the diode switches into conduction, and the capacitor rapidly discharges through the diode.
- Discharging continues until the current through the diode falls below the holding value.
- Once the current becomes below the holding value, the diode switches back to the **OFF** state, and the capacitor begins to charge again.

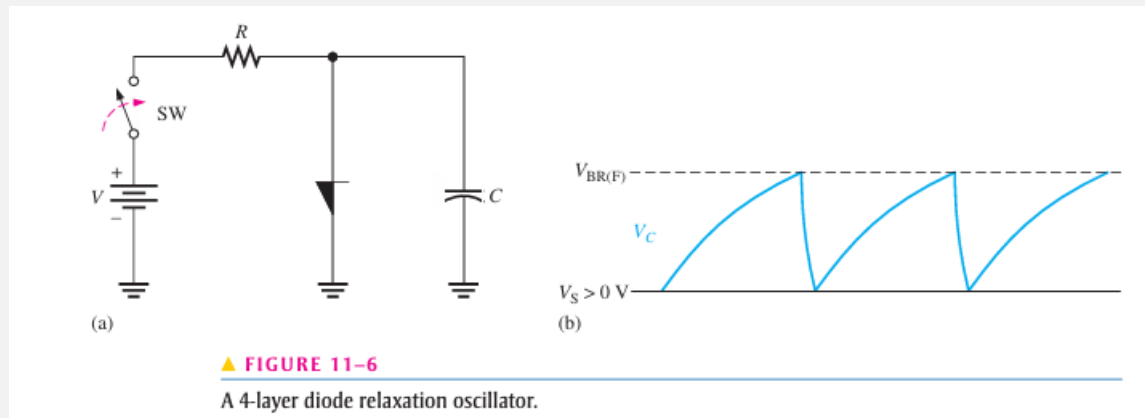


SCR (SILICON-CONTROLLED RECTIFIER)

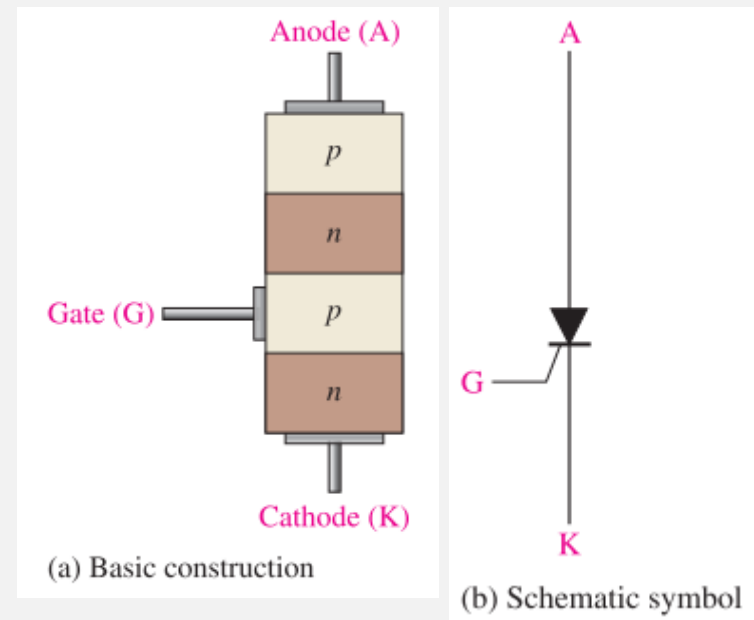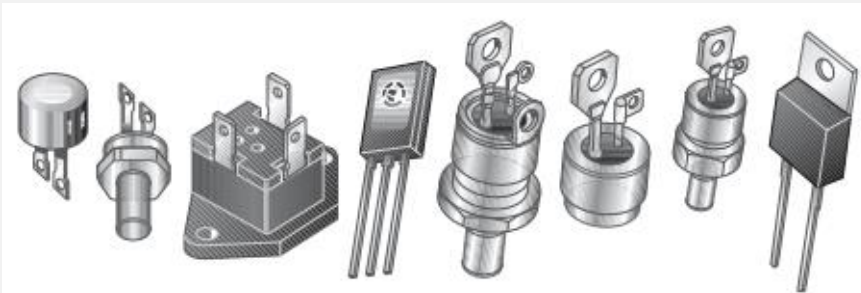- Three terminals:
 - Anode, Cathode, Gate
- Has two possible states of operation:
 - **OFF** state:
 - ❖ Acts as open circuit between anode & cathode
 - ❖ High resistance
 - **ON** state:
 - ❖ Acts ideally as a short from the anode to the cathode
 - ❖ Small on (forward) resistance




SCR EQUIVALENT CIRCUIT

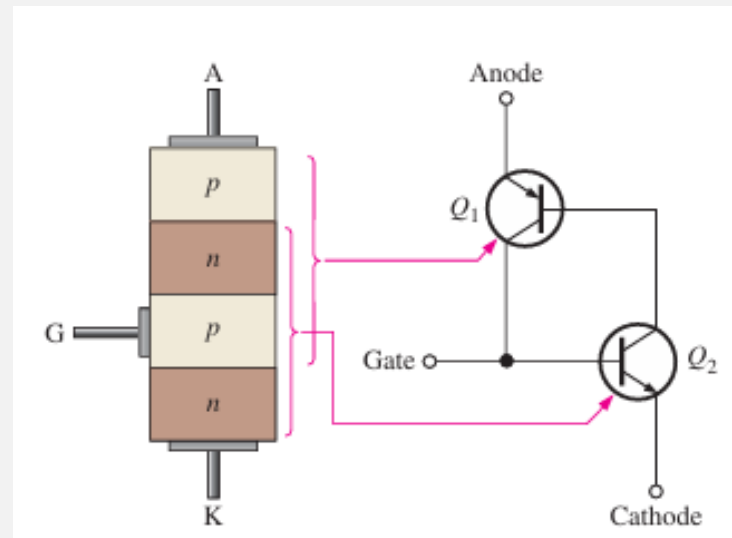- 4-layer diode except for the gate connection
- The upper *pnp* layers act as a transistor, Q_1
- The lower *nnp* layers act as a transistor, Q_2
- Two middle layers are “shared”




SCR “OFF” STATE

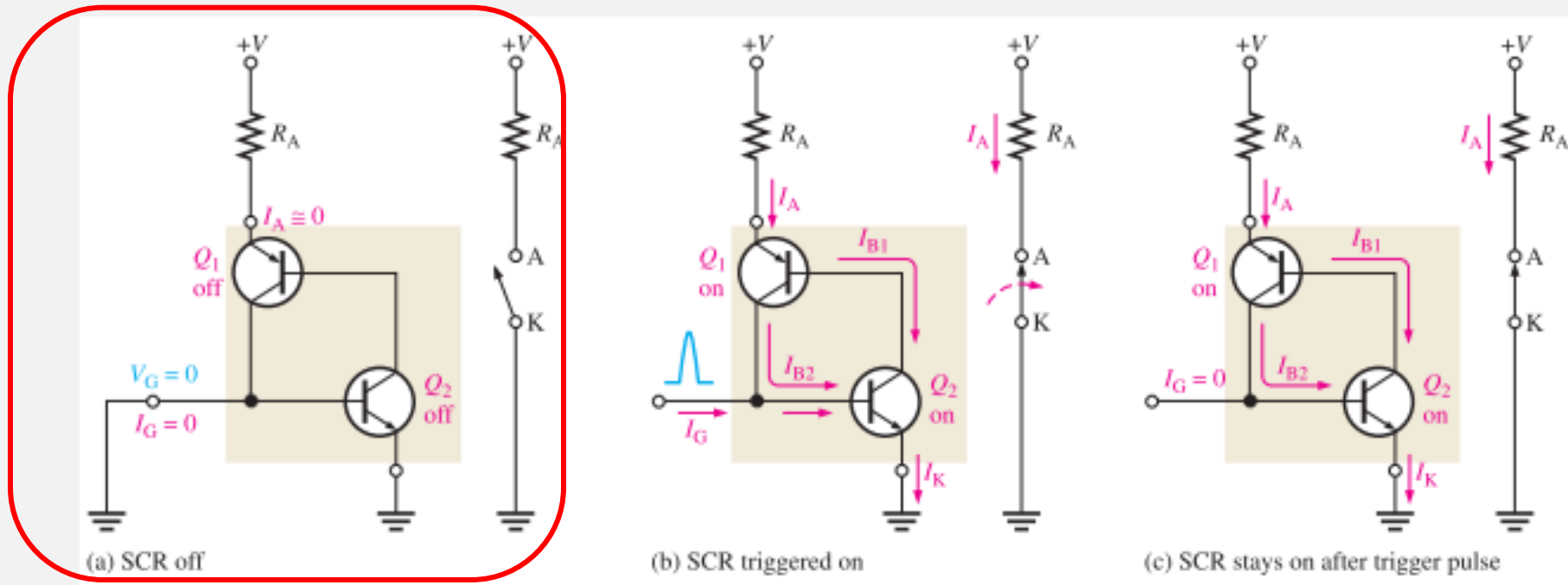


- ❖ Gate current, I_G , is zero.
- ❖ The device acts as a 4-layer diode in the **OFF** state
- ❖ Very high resistance between anode and cathode

SCR “ON” STATE

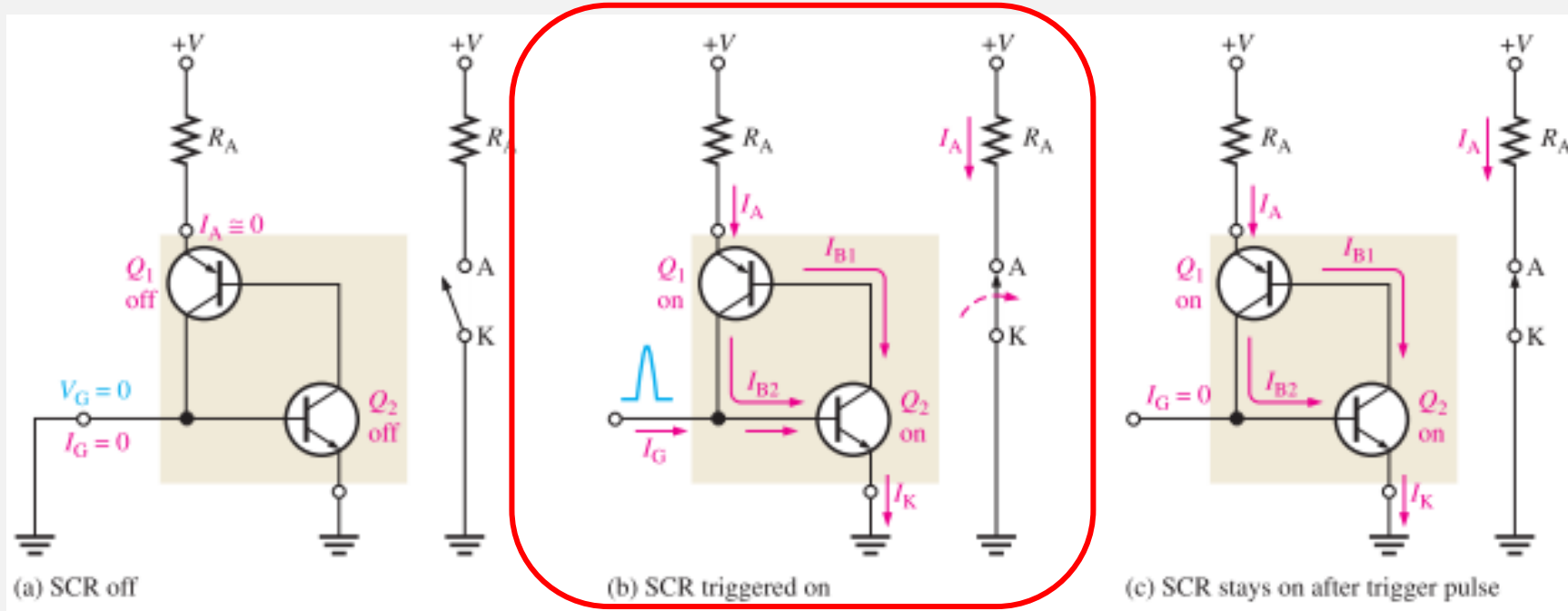

- ❖ Positive pulse of current (trigger) is applied to the gate
- ❖ Both transistors, Q_1 and Q_2 are **ON**
- ❖ I_{B2} turns on $Q_2 \rightarrow$ provides path for I_{B1} , thus turning on Q_1
- ❖ Q_1 collector's current provides additional base current for Q_2



SCR AFTER TRIGGER PULSE

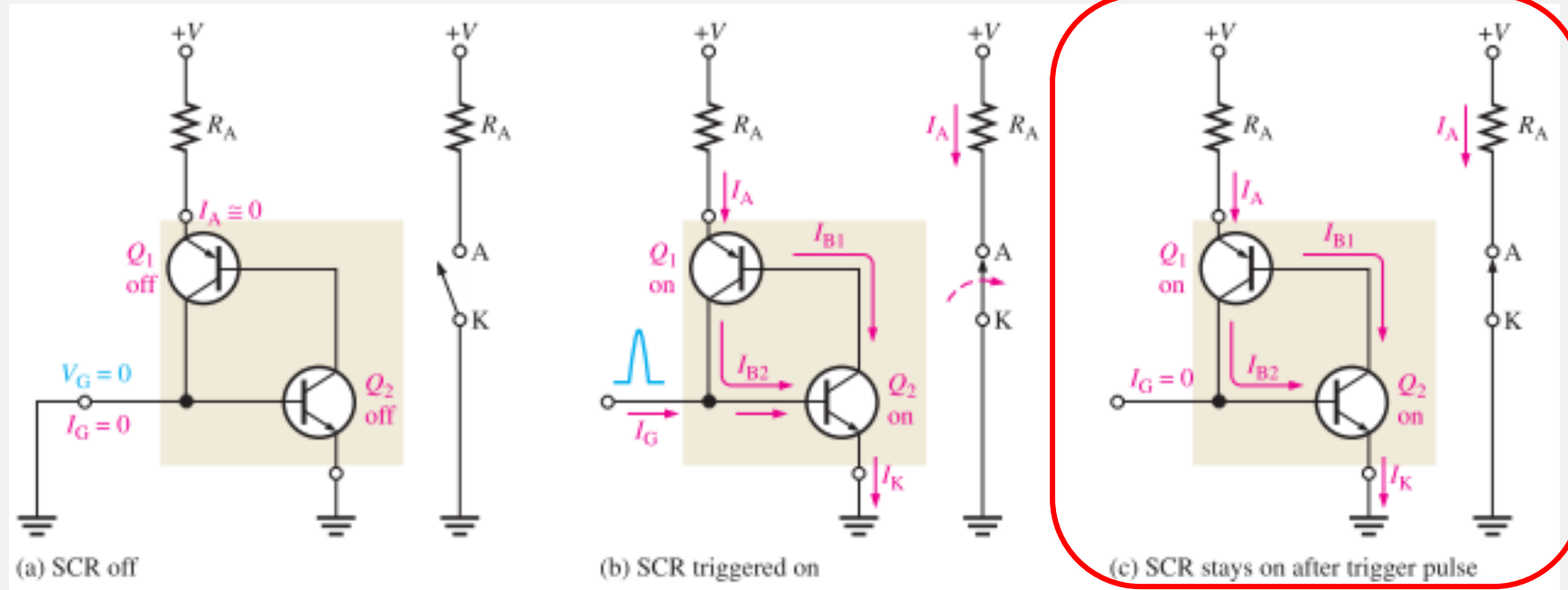

- ❖ Q_2 stays in conduction after trigger pulse is removed from the gate
- ❖ Low resistance between Anode and Cathode
- ❖ Q_2 sustains the saturated conduction of Q_1 by providing path for I_{B1}
- ❖ Q_1 sustains the saturated conduction of Q_2 by providing path for I_{B2}
- ❖ Thus, the device stays on (latches) once it is triggered on


SCR CHARACTERISTIC CURVES

- An SCR can also be turned on without gate triggering by increasing the anode-to-cathode voltage to a value exceeding the forward-breakover voltage $V_{BR(F)}$.
- The forward-breakover voltage decreases as I_G is increased above 0 A.
- Eventually, a value of I_G is reached at which the SCR turns on at a very low anode-to-cathode voltage.
- The gate current controls the value of forward breakover voltage, $V_{BR(F)}$, required for turn-on.

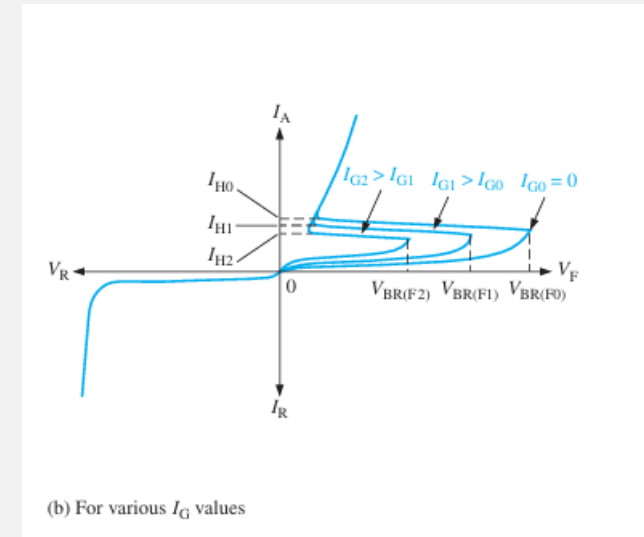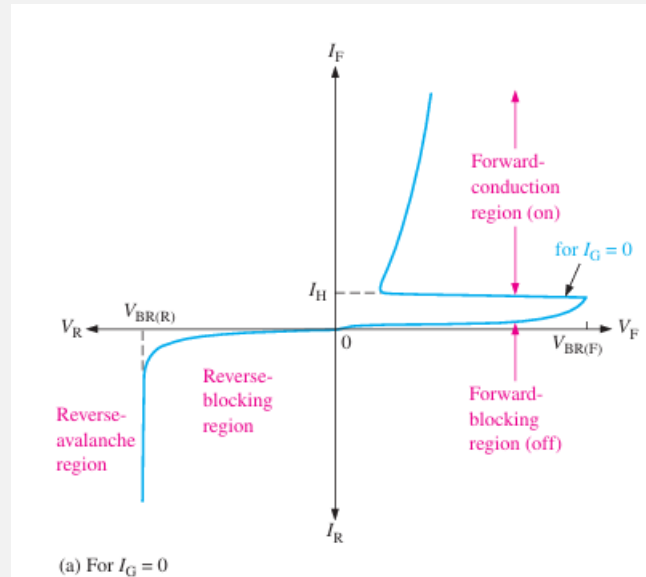

TURNING THE SCR OFF

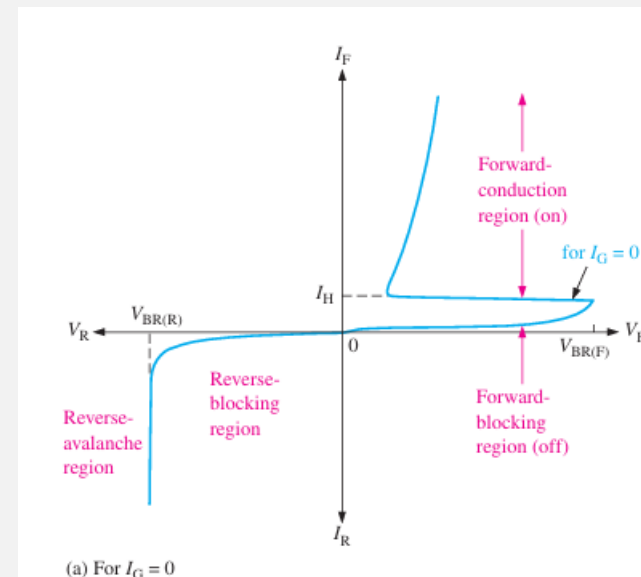
- Turning SCR off → Dropping the Anode current below the holding current (I_H)
- When the gate returns to 0V after the trigger pulse is removed, the SCR cannot turn off; it stays in the forward-conduction region.
- Two basic methods for turning off the SCR:
 1. Anode current interruption
 2. Forced commutation



TURNING THE SCR OFF

Anode current interruption:

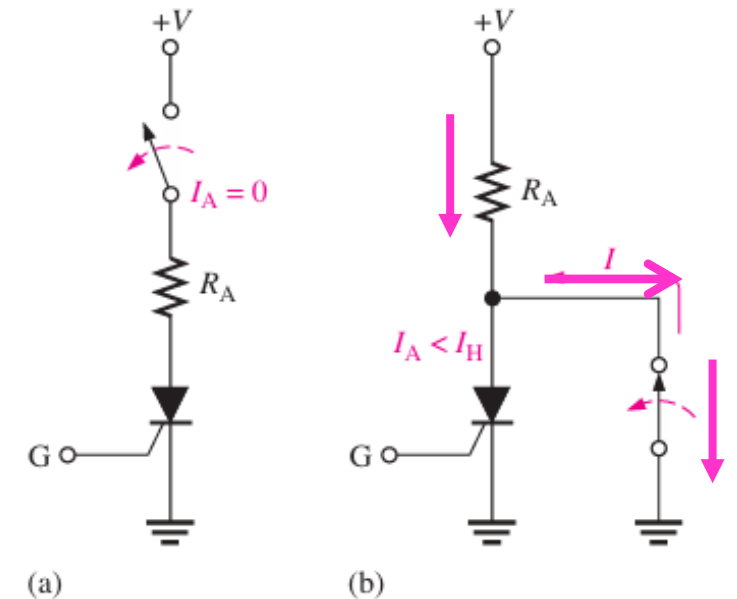
- Momentary series arrangement **(a)** – simply reduces the anode current to zero and causes the SCR to turn off
- Parallel switching arrangement **(b)** – routes part of the total current away from the SCR, thereby reducing the anode current to a value less than I_H .



TURNING THE SCR OFF

Forced Commutation

- Momentarily forcing current through SCR in the direction opposite to the forward-conduction → Net forward current is reduced below the holding value (I_H)
- The basic circuit consist of:
 - Transistor switch
 - Capacitor
- While SCR conducting the switch is open and C_c is charged to supply voltage through R_c (a)
- To turn off the SCR
 - Switch is closed
 - Placing the capacitor across the SCR and forcing current through it opposite to the forward current (b)
 - Takes few microseconds up to $30\ \mu s$

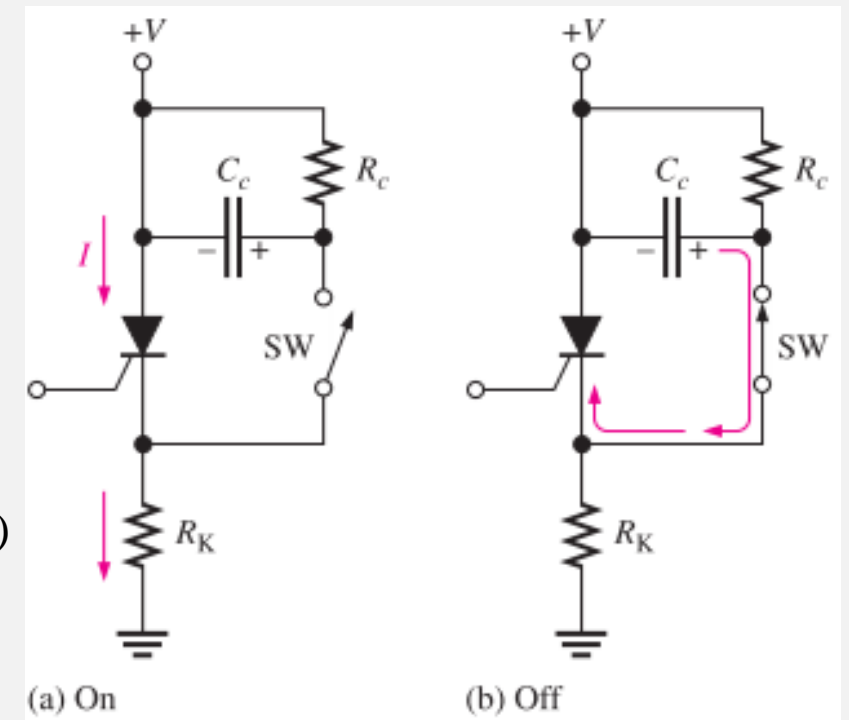


SCR CHARACTERISTICS AND RATING

❑ Forward-breakover voltage $V_{BR(F)}$

- Voltage at which the SCR enters the forward-conduction region
- $V_{BR(F)}$ is maximum when $I_G = 0$ and is designated $V_{BR(F0)}$
- When the gate current is increased, $V_{BR(F)}$ decreases and is designated $V_{BR(F1)}$, $V_{BR(F2)}$ and so on, for increasing steps in gate current (I_{G1} , I_{G2} and so on)

❑ Holding current I_H

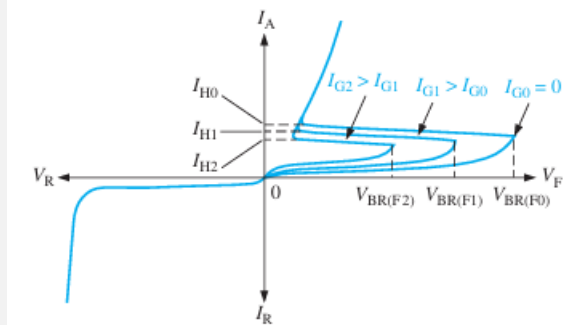- The value of anode current below which the SCR switches from forward-conduction region to the forward-blocking region
- The value increases with decreasing values of I_G and is maximum for $I_G = 0$



(b) For various I_G values

SCR CHARACTERISTICS AND RATING

❑ Gate trigger current I_{GT}

- The value of gate current necessary to switch the SCR from the forward-blocking region to the forward-conduction region under specified conditions.

❑ Average Forward current $I_{F(AVG)}$

- The maximum continuous anode current (DC) that the device can withstand in the conduction state under specified conditions.

SCR CHARACTERISTICS AND RATING

❑ Forward-blocking and reverse-blocking region

- These regions correspond to the *off* condition of the SCR where the forward current from anode to cathode is blocked by the effective open circuit of the SCR

❑ Reverse breakdown voltage ($V_{BR(F)}$)

- This parameter specifies the value of reverse voltage from cathode to anode at which the device breaks into the avalanche region and begins to conduct heavily (the same as in a *pn* junction diode).


❑ Forward-conduction region

- This region corresponds to the *on* condition of the SCR where there is forward current from anode to cathode through the very low resistance (approximate short) of the SCR.

SCR APPLICATIONS

ON-OFF CONTROL OF CURRENT


- Permits current to be switched to a load by the momentary closure of switch SW1 and removed from the load by the momentary closure of switch SW2.
- Assuming the SCR is initially off, momentary closure of SW1 provides a pulse of current out of the gate, thus triggering the SCR **on**, so that it conducts current through R_L .
- The SCR remains in conduction even after the momentary contact of SW1 is removed if the anode current is equal to or greater than the holding current, I_H .
- When SW2 is momentarily closed, current is shunted around the SCR, thus reducing its anode current below the holding value, I_H . → This turns the SCR **off** and reduces the load current to zero.

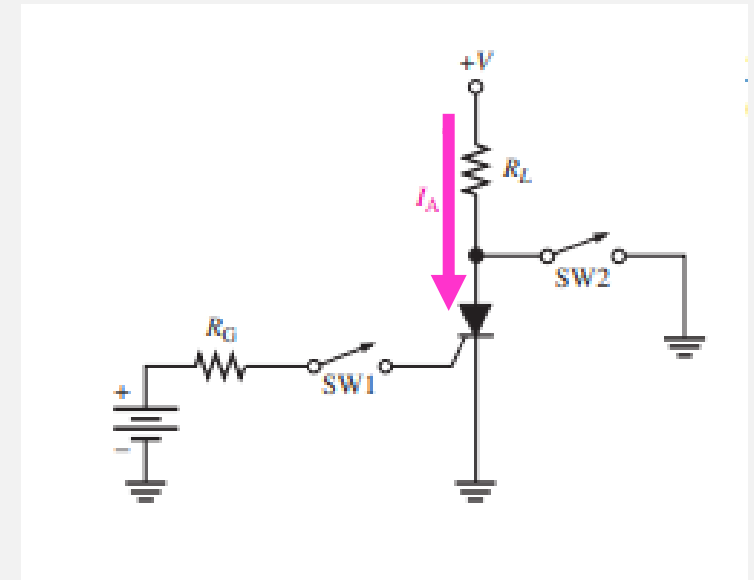

SCR APPLICATIONS

HALF-WAVE POWER CONTROL

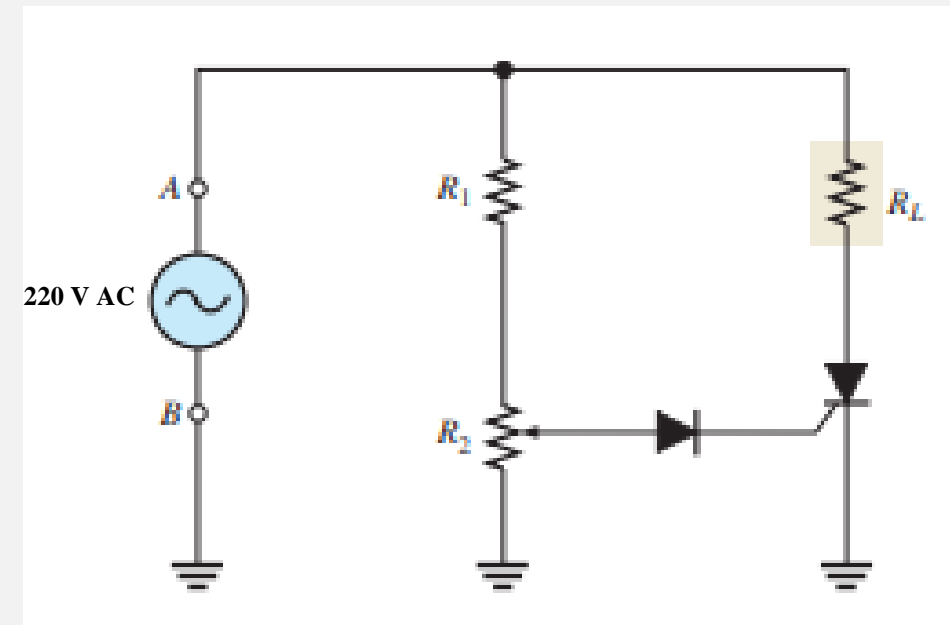- Control of AC power for lamp dimmers, electric heaters and electric motors
- R_L represents the resistance of the load
- Resistor R_1 limits the current, and potentiometer R_2 sets the trigger level for the SCR
- By adjusting R_2 , the SCR can be made to trigger at any point on the positive half-cycle of the AC waveform between 0° and 90° .




Half-wave, variable-resistance, phase-control circuit

SCR APPLICATIONS

HALF-WAVE POWER CONTROL

- When the SCR triggers near the beginning of the cycle (approximately 0°), it conducts for approximately 180° and maximum power is delivered to the load.
- When it triggers near the peak of the positive half-cycle (90°), the SCR conducts for approximately 90° and less power is delivered to the load.
- By adjusting R_2 triggering can be made to occur anywhere between these two extremes, and therefore, a variable amount of power can be delivered to the load.
- Triggering at the 45° point:
 - When the AC input goes negative, the SCR turns off and does not conduct again until the trigger point on the next positive half-cycle. The diode prevents the negative AC voltage from being applied to the gate of the SCR

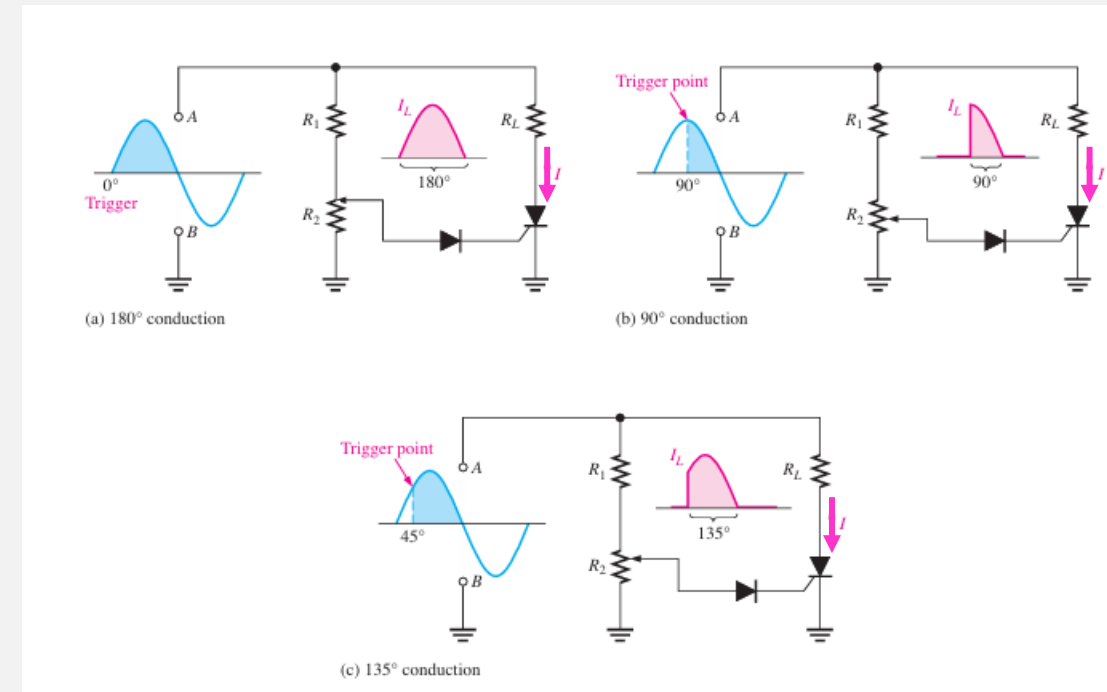

SCR APPLICATIONS

OVER-VOLTAGE PROTECTION

- The DC output voltage from the regulator is monitored by the Zener diode (D_1) and the resistive voltage divider (R_1 and R_2) .
- The upper limit of the output voltage is set by the zener voltage.
- If this voltage is exceeded, the zener conducts and the voltage divider produces an SCR trigger voltage.
- The trigger voltage turns on the SCR, which is connected across the line voltage.
- The SCR current causes the fuse to blow, thus disconnecting the line voltage from the power supply.

